
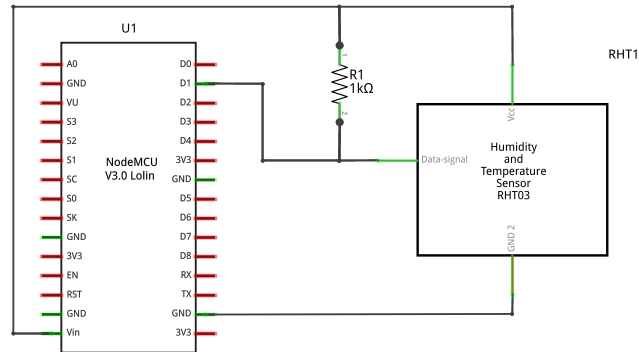


Step 1

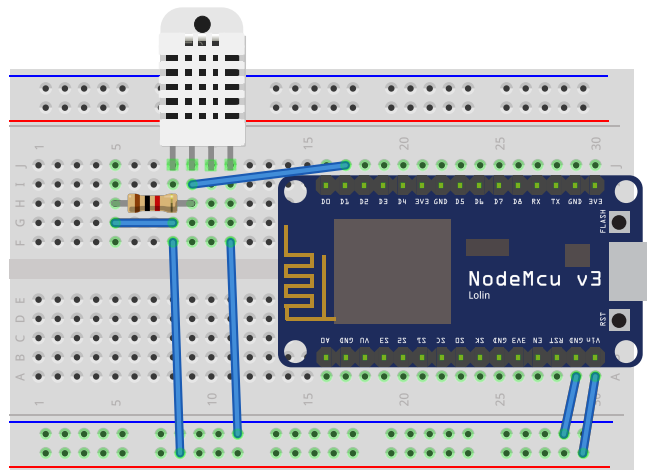Wire up this schematic on the bread board:



fritzing



fritzing